

Bachelor of Science (B.Sc.) Semester—I (C.B.S.) Examination

ELECTRONICS

(Fundamentals of Digital Electronics)

Compulsory Paper—2

Time : Three Hours]

[Maximum Marks : 50]

N.B. :— (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat and well labelled diagrams wherever necessary.

EITHER

1. (A) What is an Excess 3 code ? What are the advantages of XS3 code over 8421 code ? Express the following numbers in XS3 code :

(I) 821

(II) 2065

Add the following decimal numbers by first converting them into XS3 code.

(a) $(42)_{10} + (16)_{10}$

(b) $(84)_{10} + (56)_{10}$

(c) $(75)_{10} + (9)_{10}$

1+1+2+6

OR

- (B) Explain the method of converting decimal number to Hexadecimal with suitable example.

Convert the following :

$$(9F2)_{16} = (\quad)_8$$

$$(27.16)_{10} = (\quad)_2$$

Explain 1's complement and 2's complement subtraction method with suitable examples.

EITHER

2. For the logic expression $Y = A\bar{B} + \bar{A}B$
- Obtain the truth table
 - Name the operation performed
 - Realize this operation using AND, OR, NOT gates
 - Realize this operation using NAND gates only

Using De Morgan's theorem, solve the following equation :

$$\frac{\overline{AB} \cdot \overline{CD}}{(\overline{A} + B) + (\overline{C} + D)} = AB + CD$$

5+5

OR

Draw the logic symbol, truth table and logic equation for NOR and NAND gate and explain its working.

Explain X-NOR gate with the help of logic diagram equation and truth table. Why X-NOR gate is called an equality gate ?

3+3+3+1

EITHER

3. What is K-map ? What is minterm and maxterm in K-map ? For the logic equation $f = ABC + B\bar{C}D + \bar{A}BC$:
- Make a truth table
 - Simplify using K-map
 - Draw logic circuit for given equation. How does K map differ from the truth table ?

1+2+6+1

OR

Explain SOP and POS terms in K-map with an example. Simplify the function using K-map

$$f(ABCD) = m(0, 1, 3, 5, 6, 9, 11, 12, 13, 15)$$

4+6

EITHER

4. Explain working of 3-bit parity checker with logic diagram. Draw the logic circuit of 4-bit Adder/Subtractor circuit and explain its working with suitable example. 5+5

OR

What are MUX and DEMUX ? Draw 1 : 4 demux using logic gates and explain its working with truth table. Draw the logic circuit of full adder with truth table. 2+5+3

5. Solve any **ten** of the following :

- (i) What is radix ?
- (ii) How negative numbers are represented by 2's complement method in binary number system ?
- (iii) What is BCD code ?
- (iv) State AND laws of boolean algebra.
- (v) Give application of X-OR gate.
- (vi) State duality theorem.
- (vii) What is pair and quad of K-map ?
- (viii) What is Don't care condition in NAND gate ?
- (ix) What is rollover in K-map ?
- (x) Draw the circuit of half subtractor with truth table.
- (xi) Draw the block diagram of 4 : 1 MUX.
- (xii) What is decoder ? 1×10