

**Bachelor of Science (B.Sc.) Semester—II (C.B.S.) Examination**

**ELECTRONICS (Advanced Digital Electronics)**

**Compulsory Paper—2**

Time : Three Hours]

[Maximum Marks : 50]

**Note :—** (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat and labelled diagrams wherever necessary.

**EITHER**

1. (A) Explain the construction and working of 2-input :

- (i) CMOS NAND-gate and
- (ii) CMOS NOR-gate.

5+5

**OR**

(B) Explain the following terms, w.r. to Digital IC's :

- (i) Speed of Operation
- (ii) Fan-In
- (iii) Fan-out
- (iv) Noise Immunity
- (v) Power Dissipation.

2+2+2+2+2

**EITHER**

2. (A) Explain the limitations of RS Flip-Flop. Draw and explain with logic diagram, the clocked RS Flip-Flop using NAND-gates and write its Truth Table.

2+8

**OR**

(B) What is Race-Around-Condition in a JKFF ? List different methods for avoiding Race-Around-Condition. Draw the logic diagram of JKMS flip-flop and explain its working in brief.

2+2+6

**EITHER**

3. (A) Draw the logic diagram of 4-bit ring counter and explain its working.

List the point of differences between ring counter and Johnson counter.

6+4

**OR**

(B) What is down counter ? Draw the logic diagram of 3-bit ripple down counter and explain its working with truth table and timing diagrams. List any two applications of down counter.

1+8+1

**EITHER**

4. (A) Explain the necessity of memory organization. Explain in brief, the expansion of  $16 \times 4$  memory to  $16 \times 8$  bit memory. 2+8

**OR**

(B) Draw the logic diagram of 4-bit SIPO shift register and explain its working. Explain the significance of shifting of data either to the left or to the right by 1-bit position. 8+2

5. Solve any **ten** :

- (i) What is tri-state logic ?
- (ii) Write any two features of CMOS logic.
- (iii) Define propagation delay.
- (iv) Explain the forbidden state in RSFF.
- (v) Draw the logic symbol of DFF.
- (vi) Why PRESET and CLEAR terminals are called asynchronous inputs ?
- (vii) On what factor, does the modulus of a counter depend ?
- (viii) Which condition of flip-flop is used in the construction of counter ?
- (ix) What will be the modulus of 3-bit ring counter ?
- (x) What is RAM ?
- (xi) How many IC chip of  $16 \times 4$  memory is required for the construction of  $32 \times 4$  memory chips ?
- (xii) List the advantages of bipolar memory. 1×10