

**Bachelor of Science (B.Sc.) Semester—II (C.B.S.) Examination**

**ELECTRONICS**

**(Advanced Digital Electronics)**

**Compulsory Paper—2**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :—** (1) All questions are compulsory and carry equal marks.

(2) Draw neat and well labelled diagrams wherever necessary.

**EITHER**

1. (A) Explain the working of TTL NAND gate with suitable diagram.

Define the terms :

- (i) Propagation delay
- (ii) Power consumption
- (iii) Noise immunity
- (iv) Fan-in
- (v) Fan-out.

5+5

**OR**

(B) What is tristate logic ? Explain with the help of a neat diagram, the construction and working of a TTL tristate switch.

Explain the working of CMOS NOR gate with diagram.

5+5

**EITHER**

2. (A) Draw the logic diagram of clocked SRFF using NAND gates and explain its working.

State the limitation of SRFF. How is it eliminated in D-Flip-Flop.

6+4

**OR**

(B) What is Race-Around condition in JKFF ?

How is it eliminated ?

Draw and explain the construction and working of JKMSFF.

2+1+7

**EITHER**

3. (A) Explain the construction and working of 4-bit ripple counter. State the limitations of ripple counter. 8+2

**OR**

(B) What is modified counter ? Explain the construction and working of Decade counter using JKMSFF. 2+8

**EITHER**

4. (A) What is shift register ? What are the different types of shift registers ? Explain the working of any one of them with logic diagram. 2+2+6

**OR**

(B) Draw and explain the block diagram of memory.

Construct  $16 \times 8$  memory using  $16 \times 4$  memory chips. 5+5

5. Attempt any **ten** :

(A) What is operating temperature of IC ?  
(B) State any two advantages of CMOS over TTL logic.  
(C) Give the full form of CMOS.  
(D) What is edge triggering in FF ?  
(E) Why is it necessary to have PRESET and CLEAR inputs in FFS ?  
(F) What is CLOCK ?  
(G) Draw MOD-4 counter using JKMSFF.  
(H) What is ring counter ?  
(I) How many flip-flops are required for the construction of MOD-5 counter ?  
(J) What is meant by Buffer register ?  
(K) Write any two differences between RAM and ROM.  
(L) How many memories of size  $512 \times 8$  are required to construct a memory size of  $2k \times 8$  ?

$1 \times 10 = 10$